

BỘ CÔNG THƯƠNG
ĐẠI HỌC CÔNG NGHIỆP TP. HỒ CHÍ MINH



Bài giảng

KỸ THUẬT ĐIỆN – ĐIỆN TỬ
ELECTRICITY AND ELECTRONICS

Lecturer : Le Ngoc Tran, PhD

Email : lengoctran@iuh.edu.vn

Chapter 4: Phân tích mạch AC



Introduction of AC circuit



Average Power, Apparent Power and Power Factor



Complex Power



Polyphase circuits



Single-Phase Three-Wire Systems




Three-Phase Y-Y Connection



Power Measurement

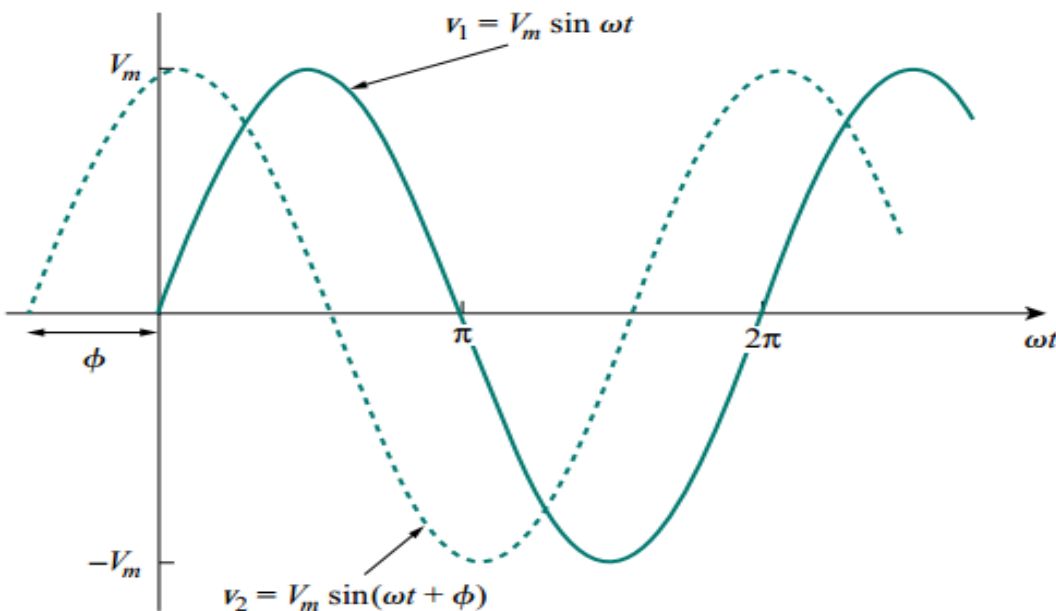4.1. Giới thiệu mạch AC

- Mạch điện mà nguồn áp hoặc nguồn dòng biến đổi theo thời gian được kích thích bởi một nguồn sine hoặc cosin thì được gọi là mạch xoay chiều AC.



$$v(t) = V_m \sin \omega t$$

V_m = the *amplitude* of the sinusoid
 ω = the *angular frequency* in radians/s
 ωt = the *argument* of the sinusoid

4.1. Giới thiệu mạch AC

❖ Biểu diễn tín hiệu điện áp hay dòng điện theo dạng hàm SINE

$$v(t) = V_m \sin \omega t$$

T được gọi là chu kỳ (period)

$$T = \frac{2\pi}{\omega} \quad \rightarrow \quad \omega T = 2\pi$$

f (Hz) là tần số (frequency)

$$f = \frac{1}{T} \quad \rightarrow \quad \omega = 2\pi f$$

ω (rad/s); ωt : argument; $(\omega t + \Phi)$: argument & Φ in the phase


$$v(t) = V_m \sin(\omega t + \phi)$$

$v(t)$ repeats itself every T seconds is shown by replacing t by $(t + T)$

$$v(t + T) = V_m \sin \omega(t + T) = V_m \sin \omega \left(t + \frac{2\pi}{\omega} \right)$$

$$v(t + T) = v(t)$$
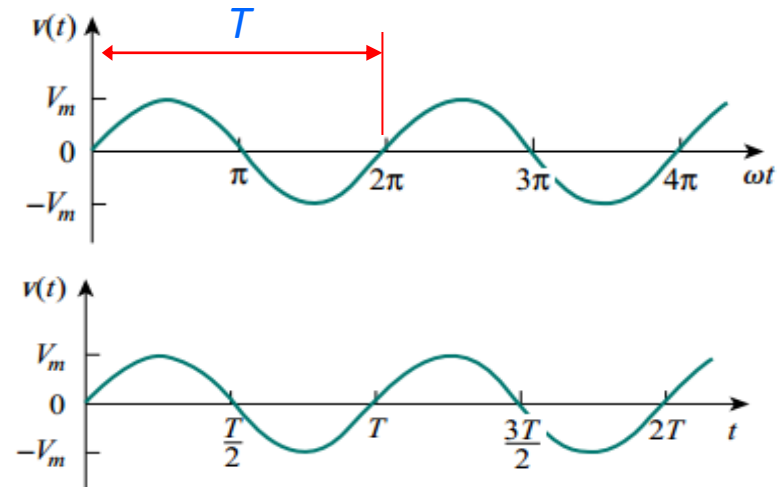
$$= V_m \sin(\omega t + 2\pi) = V_m \sin \omega t = v(t)$$



4.1. Introduction of AC circuit

❖ Sức cản của các phần tử trong mạch điện (Trở kháng- IMPEDANCE)

- Mối quan hệ giữa Điện áp – Dòng điện của các phần tử thụ động điện passive elements là:

$$V = RI, \quad V = j\omega LI, \quad V = \frac{I}{j\omega C}$$

- Viết lại theo dạng điện áp pha và dòng pha

$$\frac{V}{I} = \overset{\substack{\uparrow \\ Z_R}}{R}, \quad \frac{V}{I} = \overset{\substack{\uparrow \\ Z_L}}{j\omega L}, \quad \frac{V}{I} = \frac{1}{j\omega C} \overset{\substack{\uparrow \\ Z_C}}{}$$

- Biểu diễn định luật Ohm theo dạng pha cho các phần tử thụ động điện

$$Z = \frac{V}{I} \quad \text{or} \quad V = ZI$$


Trong đó: **Z** được gọi là trở kháng (*impedance*), đo bằng ohms.

4.1. Introduction of AC circuit

❖ Cách biểu diễn tín hiệu điện áp theo miền thời gian và dạng pha

$$v(t) = V_m \cos(\omega t + \phi) \quad \Longleftrightarrow \quad \mathbf{V} = V_m \angle \phi$$

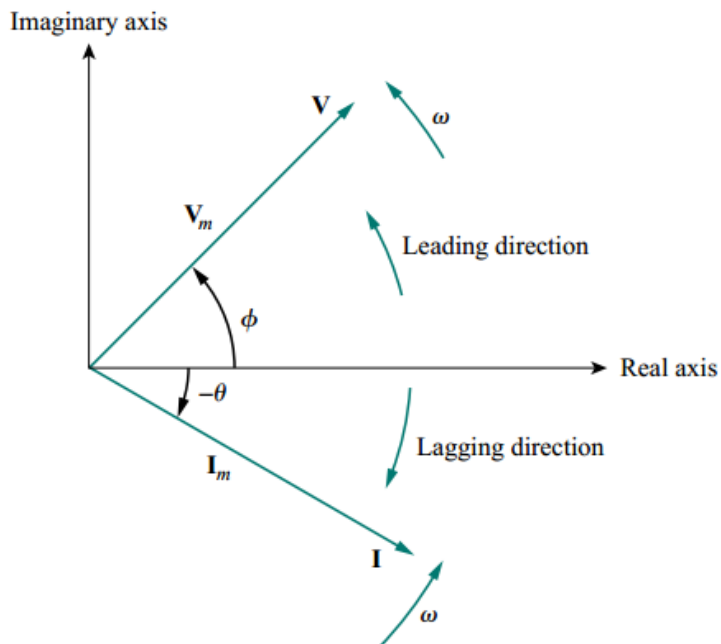(Time-domain representation) (Phasor-domain representation)




Sinusoid-phasor transformation.	
Time-domain representation	Phasor-domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

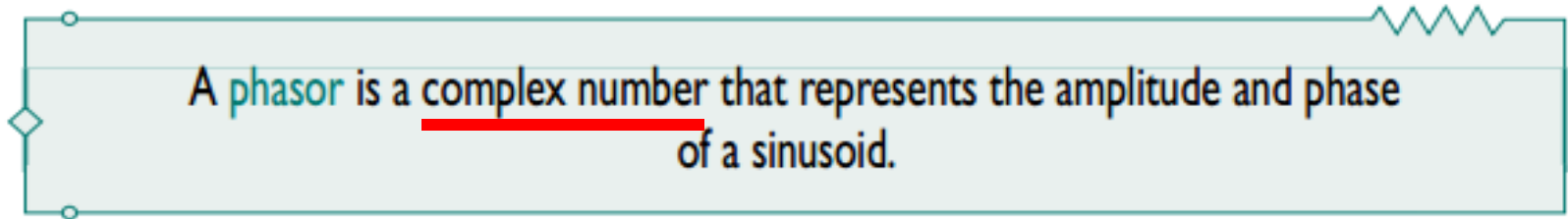4.1. Introduction of AC circuit

❖ BIỂU DIỄN TÍN HIỆU THEO DẠNG PHA

Sinusoids are easily expressed in terms of phasors, which are more convenient to work with than sine and cosine functions.



- A complex number z can be written in rectangular form as

$$z = x + jy$$

where $j = \sqrt{-1}$; x is the real part of z ; y is the imaginary part of z .

- The complex number z can also be written in polar or exponential form as

$$z = r \angle \phi = re^{j\phi}$$

where r is the magnitude of z , and ϕ is the phase of z .

4.1. Introduction of AC circuit

❖ BIỂU DIỄN IMPEDANCE THEO DẠNG PHA

- The impedance may be expressed in rectangular form as

$$\mathbf{Z} = R + jX$$

Resistance (Trở kháng) ↑
↓ Reactance (Điện kháng)

Impedances and admittances of passive elements.

Element	Impedance	Admittance
R	$\mathbf{Z} = R$	$\mathbf{Y} = \frac{1}{R}$
L	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = \frac{1}{j\omega L}$
C	$\mathbf{Z} = \frac{1}{j\omega C}$	$\mathbf{Y} = j\omega C$

Where:

- $R = \text{Re } \mathbf{Z}$ is the *resistance* and $X = \text{Im } \mathbf{Z}$ is the *reactance*.
- The reactance X may be positive or negative. (impedance is inductive when X is positive or capacitive when X is negative).
- Impedance $\mathbf{Z} = R + jX$ is said to be inductive or lagging since current lags voltage, while impedance $\mathbf{Z} = R - jX$ is capacitive or leading because current leads voltage.
- The impedance, resistance, and reactance are all measured in ohms

4.1. Introduction of AC circuit

❖ BIỂU DIỄN IMPEDANCE THEO DẠNG PHA

Expression of Impedance

$$\mathbf{Z} = R + jX = |\mathbf{Z}| \angle \theta$$

Polar form


$$\mathbf{Z} = |\mathbf{Z}| \angle \theta$$

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

$$R = |\mathbf{Z}| \cos \theta, \quad X = |\mathbf{Z}| \sin \theta$$

4.2. Công suất của nguồn xoay chiều-CS tức thời

Instantaneous Power (công suất tức thời)

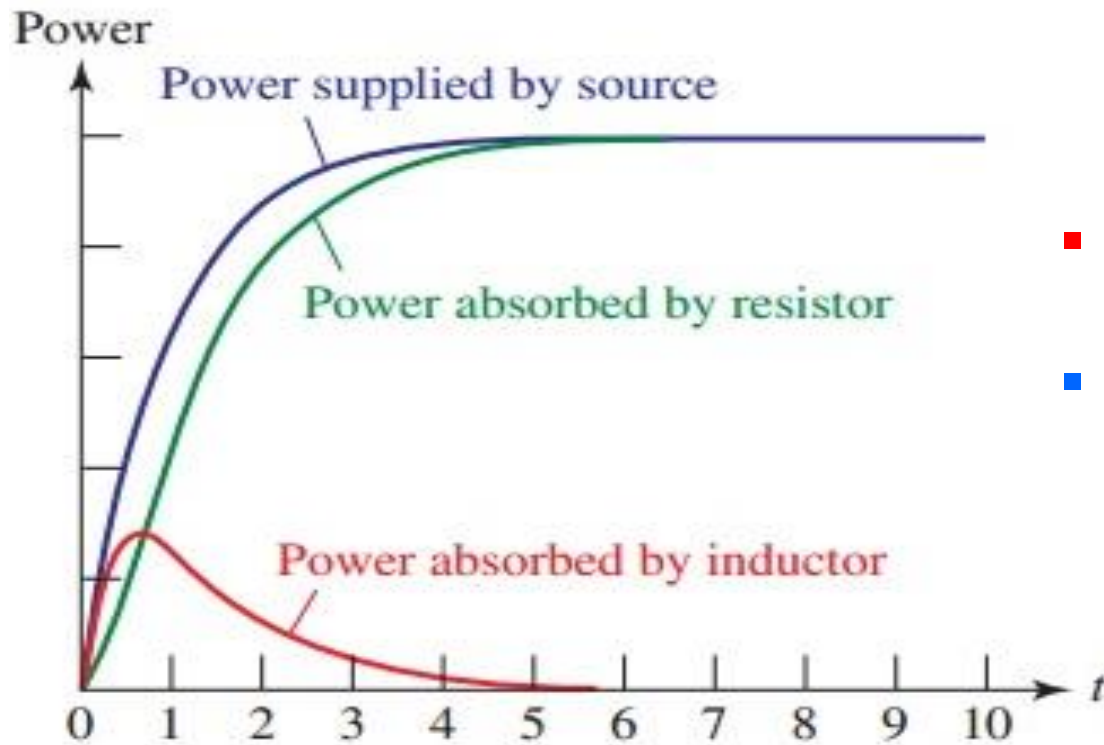

- $p(t) > 0$, power is absorbed by the circuit.
- $p(t) < 0$, power is absorbed by the source;

Power is transferred from the circuit to the source. This is possible because of the storage elements (capacitors and inductors) in the circuit.

4.2. Instantaneous Power – Công suất tức thời

Instantaneous Power

$$p(t) = v(t)i(t) \quad (3.1)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

where V_m and I_m are the amplitudes (or peak values), and θ_v and θ_i are the phase angles of the voltage and current, respectively.


$$\cos A \cos B = \frac{1}{2} [\cos(A - B) + \cos(A + B)]$$

$$\rightarrow p(t) = v(t)i(t) = V_m I_m \underbrace{\cos(\omega t + \theta_v)}_A \underbrace{\cos(\omega t + \theta_i)}_B \quad (3.2)$$

$$\rightarrow p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \quad (3.3)$$

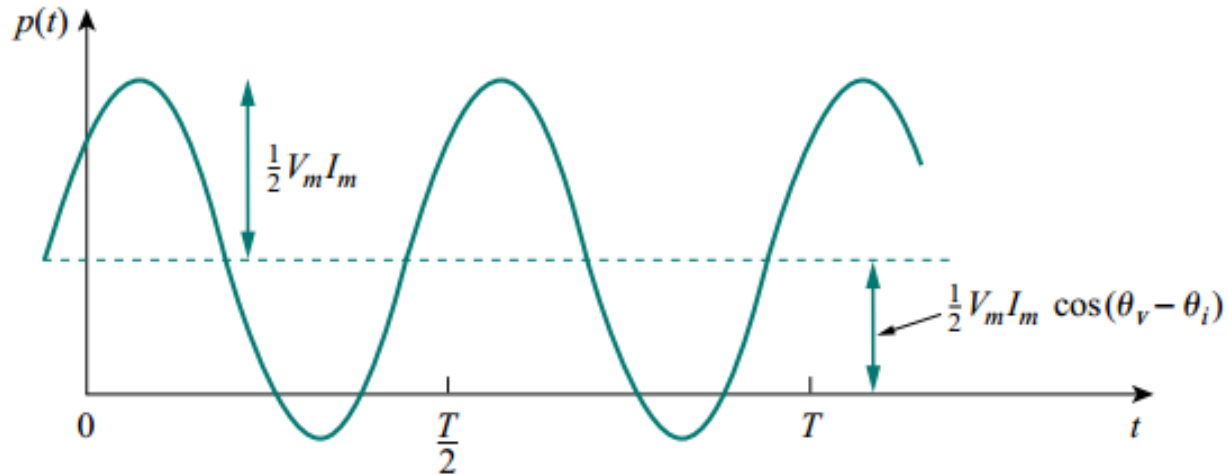4.3 Average Power- công suất trung bình

- Instantaneous Power:
$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$



The instantaneous power changes with time and is therefore difficult to measure. => The average power is more convenient to measure.

□ Definition:

The average power is the average of the instantaneous power over one period

The **wattmeter**, the instrument for measuring **average power**

4.3 Average Power- công suất trung bình

□ Demonstrate:

- Instantaneous Power: $p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$

- Average power: $P = \frac{1}{T} \int_0^T p(t) dt$

$$\Rightarrow P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt}_{\text{integrand is constant}} + \underbrace{\frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt}_{\text{integrand is a sinusoid}}$$

- Average power:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

4.3 Average Power- công suất trung bình

- *Average power:*


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

- When $\theta_v = \theta_i$, the **voltage** and **current** are **in phase**, purely resistive circuit or resistive load R

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |\mathbf{I}|^2 R$$

- When $\theta_v - \theta_i = \pm 90^\circ$, we have a **purely reactive circuit**, and
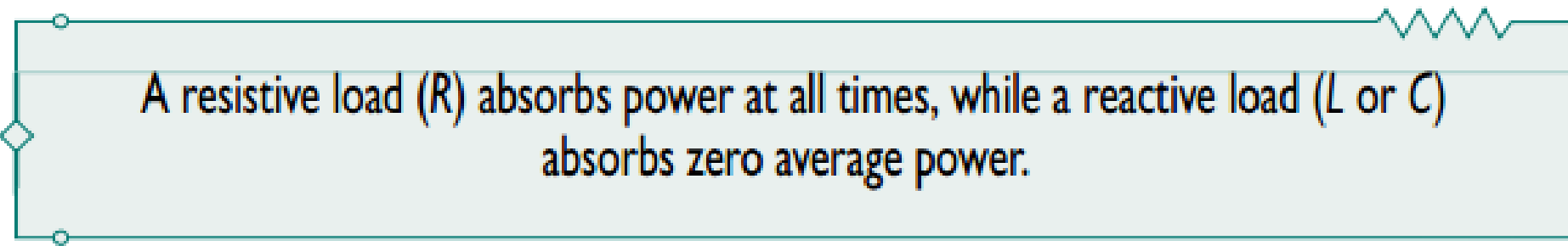
$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$



A resistive load (R) absorbs power at all times, while a reactive load (L or C) absorbs zero average power.

Exercise 3.6

Given that $v(t) = 120 \cos(377t + 45^\circ)$ V and $i(t) = 10 \cos(377t - 10^\circ)$ A. Find the **instantaneous power** and the **average power** absorbed by the passive linear network.

4.3 Average Power- công suất trung bình

Solution Ex 3.6:

$$\begin{cases} v(t) = 120 \cos(377t + 45^\circ) \text{ V} \\ i(t) = 10 \cos(377t - 10^\circ) \text{ A} \end{cases}$$

- The instantaneous power:

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\rightarrow p(t) = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

- The average power:

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} 120(10) \cos[45^\circ - (-10^\circ)] \\ &= 600 \cos 55^\circ = 344.2 \text{ W} \end{aligned}$$

Exercise 3.7

Calculate the average power absorbed by an impedance $\mathbf{Z} = 30 - j70 \, \Omega$

when a voltage $\mathbf{V} = 120 \angle 0^\circ$ is applied across it.

Solution Ex3.7:

The current through the impedance is

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = 1.576 \angle 66.8^\circ \text{ A}$$


The average power is

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ) = 37.24 \text{ W}$$

4.3 Average Power- công suất trung bình

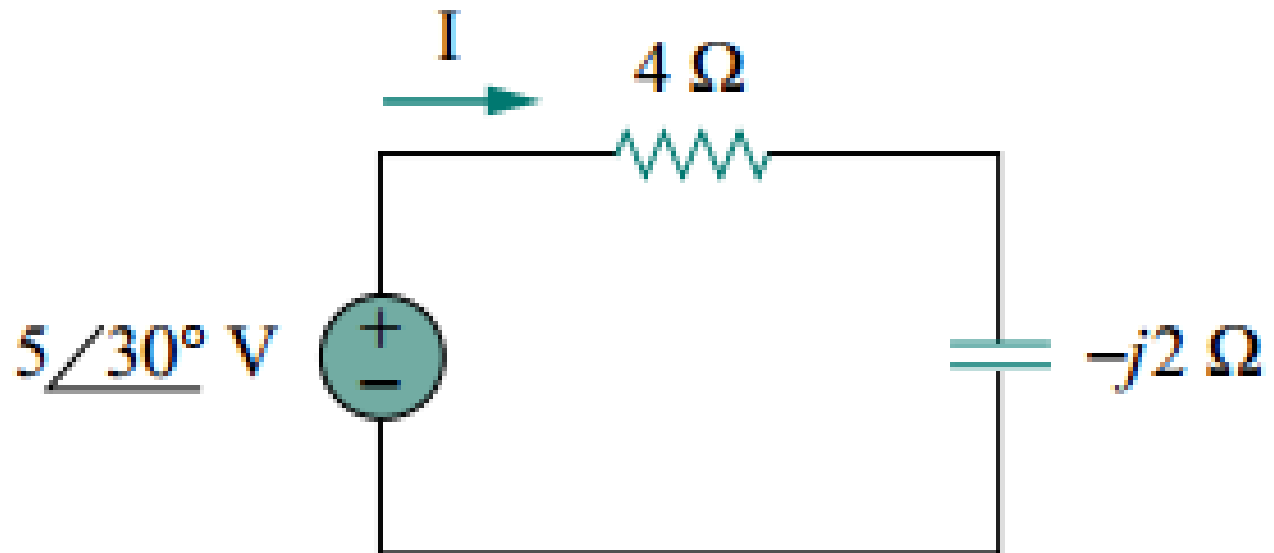Exercise 3.8

For the circuit shown in Figure, find the average power supplied by the source and the average power absorbed by the resistor.



4.3 Average Power- công suất trung bình

Solution:

The current \mathbf{I} is given by

$$\mathbf{I} = \frac{5 \angle 30^\circ}{4 - j2} = \frac{5 \angle 30^\circ}{4.472 \angle -26.57^\circ} = 1.118 \angle 56.57^\circ \text{ A}$$

The average power supplied by the voltage source is

$$P = \frac{1}{2}(5)(1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$

The current through the resistor is

$$\mathbf{I} = \mathbf{I}_R = 1.118 \angle 56.57^\circ \text{ A}$$

and the voltage across it is

$$\mathbf{V}_R = 4\mathbf{I}_R = 4.472 \angle 56.57^\circ \text{ V}$$

The average power absorbed by the resistor is

$$P = \frac{1}{2}(4.472)(1.118) = 2.5 \text{ W}$$

which is the same as the average power supplied. Zero average power is absorbed by the capacitor.

4.3 Average Power- công suất trung bình

HOMEWORK 3.4

Calculate the instantaneous power and average power absorbed by the passive linear network of Fig.

$$v(t) = 80 \cos(10t + 20^\circ) \text{ V} \quad \text{and} \quad i(t) = 15 \sin(10t + 60^\circ) \text{ A}$$


Answer: $385.7 + 600 \cos(20t - 10^\circ) \text{ W}$, 385.7 W .

HOMEWORK 3.5

A current $\mathbf{I} = 10 \angle 30^\circ$ flows through an impedance $\mathbf{Z} = 20 \angle -22^\circ \Omega$. Find the average power delivered to the impedance.

Answer: 927.2 W .

HOMEWORK 3.6

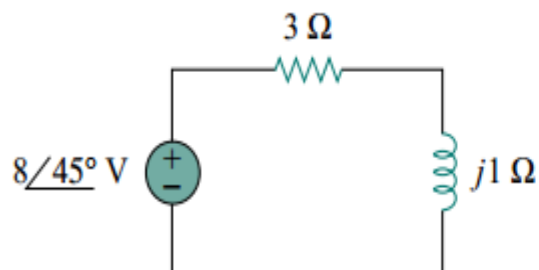



In the circuit of Fig. 11.4, calculate the average power absorbed by the resistor and inductor. Find the average power supplied by the voltage source.

Answer: 9.6 W , 0 W , 9.6 W .

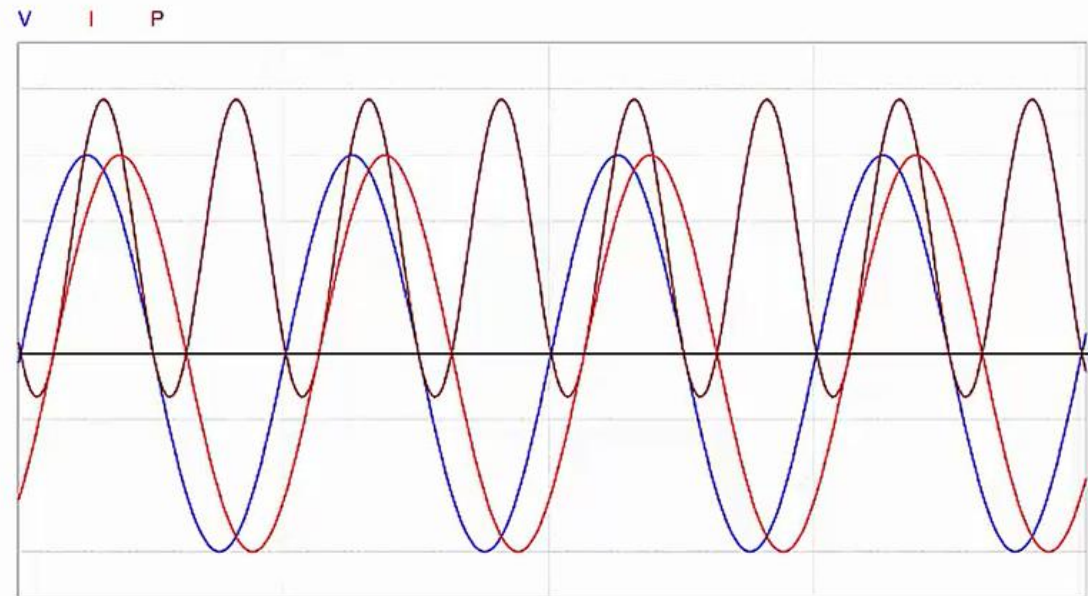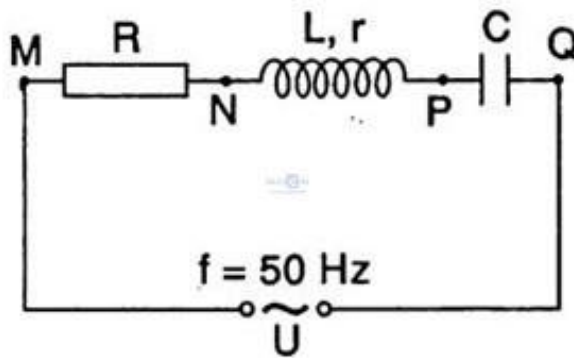4.4 Apparent Power and Power Factor

REAL, REACTIVE, AND APPARENT POWER:

- Power in system with resistive and reactive components*



- REAL** -> **Resistive (R)**
- REACTIVE** -> **L, C: Oscillates**

Apparent power (S): Công suất biểu kiến

Power Factor (PF): Hệ số công suất

4.4 Apparent Power and Power Factor

- Instantaneous Power:** $p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$

- Average power:** $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

$\Rightarrow P = \frac{1}{\sqrt{2}} V_m \frac{1}{\sqrt{2}} I_m \cos(\theta_v - \theta_i) = \underbrace{0.707 * V_m}_{V_{rms}} * \underbrace{0.707 * I_m}_{I_{rms}} \cos(\theta_v - \theta_i)$

- Other terms of the power values**


$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

$$S = V_{rms} I_{rms}$$

Apparent power S

$$\cos(\theta_v - \theta_i)$$

power factor (pf)

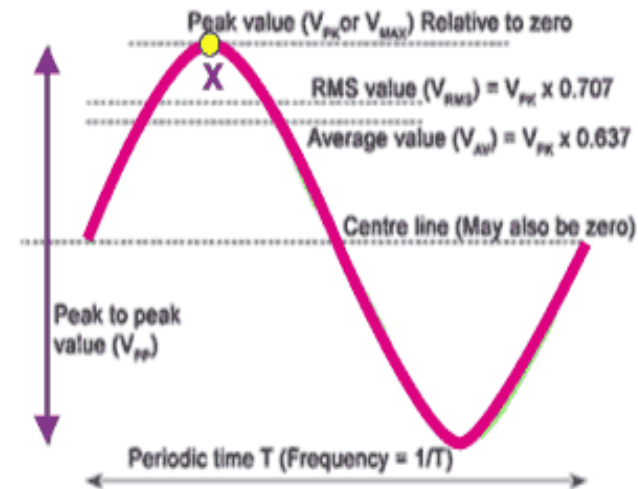


The **apparent power** (in VA) is the product of the rms values of voltage and current.

4.5 Complex Power- Công suất phức

- Complex power is important in power analysis because it contains **all the information** pertaining to the power absorbed by a given load.

$$S = V_{\text{rms}} I_{\text{rms}}^*$$

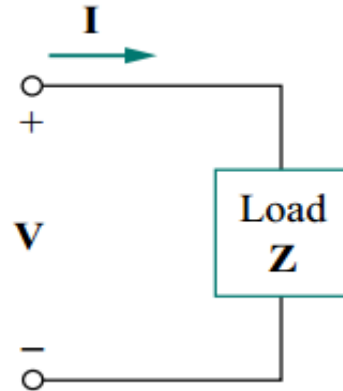

$$Z = \frac{V}{I} = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \angle \theta_v - \theta_i$$

$$V_{\text{rms}} = Z I_{\text{rms}}$$

$$S = I_{\text{rms}}^2 Z = \frac{V_{\text{rms}}^2}{Z^*}$$

Since $Z = R + jX$,


$$S = I_{\text{rms}}^2 (R + jX) = P + jQ$$

- The magnitude of the complex power is the **apparent power**
- The complex power is measured in volt-amperes (VA)
- The angle of the complex power is the **power factor** angle.

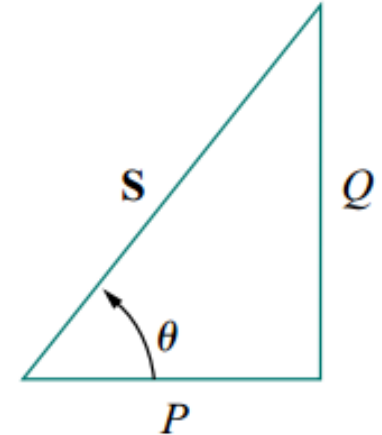4.5 Complex Power- Công suất phức

Complex power (in VA) is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. As a complex quantity, its real part is real power P and its imaginary part is reactive power Q .

$$\mathbf{S} = I_{\text{rms}}^2 (R + jX) = P + jQ$$



where P and Q are the real and imaginary parts of the complex power

$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R$$

$$Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

- P is the average or real power and it depends on the load's resistance R
- Q depends on the load's reactance X and is called the reactive power.

4.5 Complex Power- Công suất phức


- **Average power (P):** $P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i),$

It is real power (P) in watts delivered to a load; it is the only useful power. It is the actual power dissipated by the load.

- **Reactive power (Q):** $Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$

- It is a measure of the energy exchange between the source and the reactive part of the load.
- The unit of Q is the *volt-ampere reactive* (VAR) to distinguish it from the real power
- The reactive power is being transferred back and forth between the load and the source. It represents a lossless interchange between the load and the source.
 1. $Q = 0$ for resistive loads (unity pf).
 2. $Q < 0$ for capacitive loads (leading pf).
 3. $Q > 0$ for inductive loads (lagging pf).



4.5 Complex Power- Công suất phức

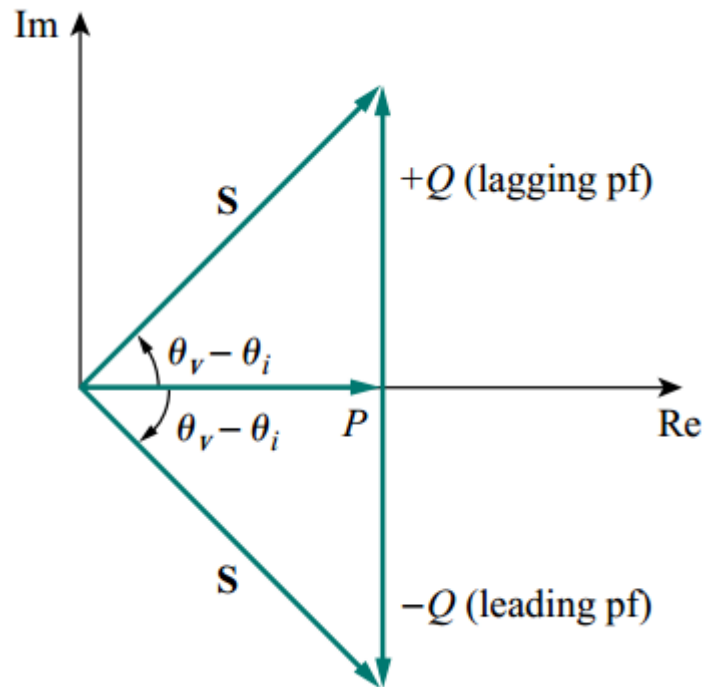

- When **S** lies in the first quadrant, we have an inductive load and a lagging PF
- When **S** lies in the fourth quadrant, the load is capacitive and the PF is leading

It is also possible for the complex power to lie in the second or third quadrant. This requires that the load impedance have a negative resistance, which is possible with active circuits.

4.5 Complex Power- Công suất phức

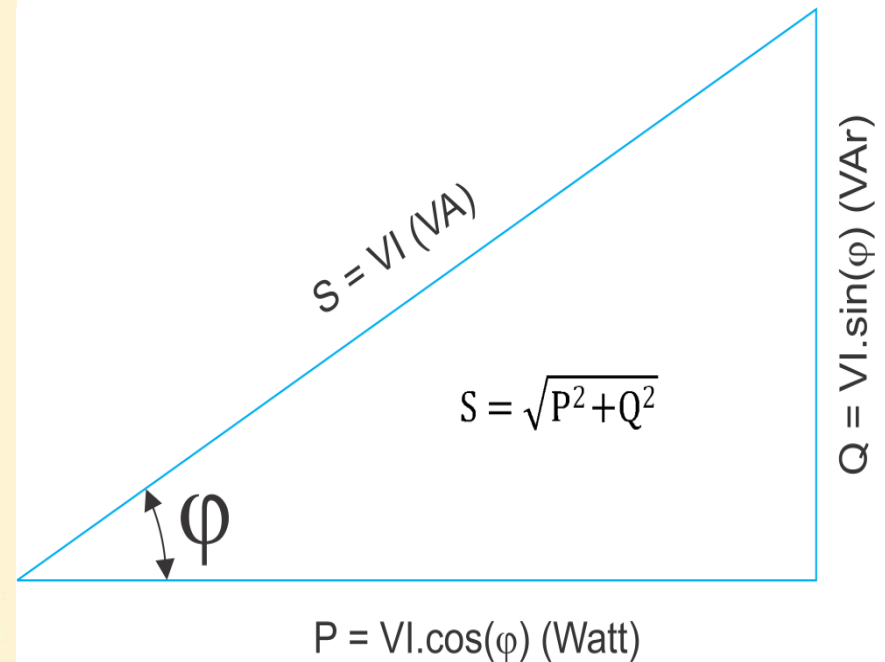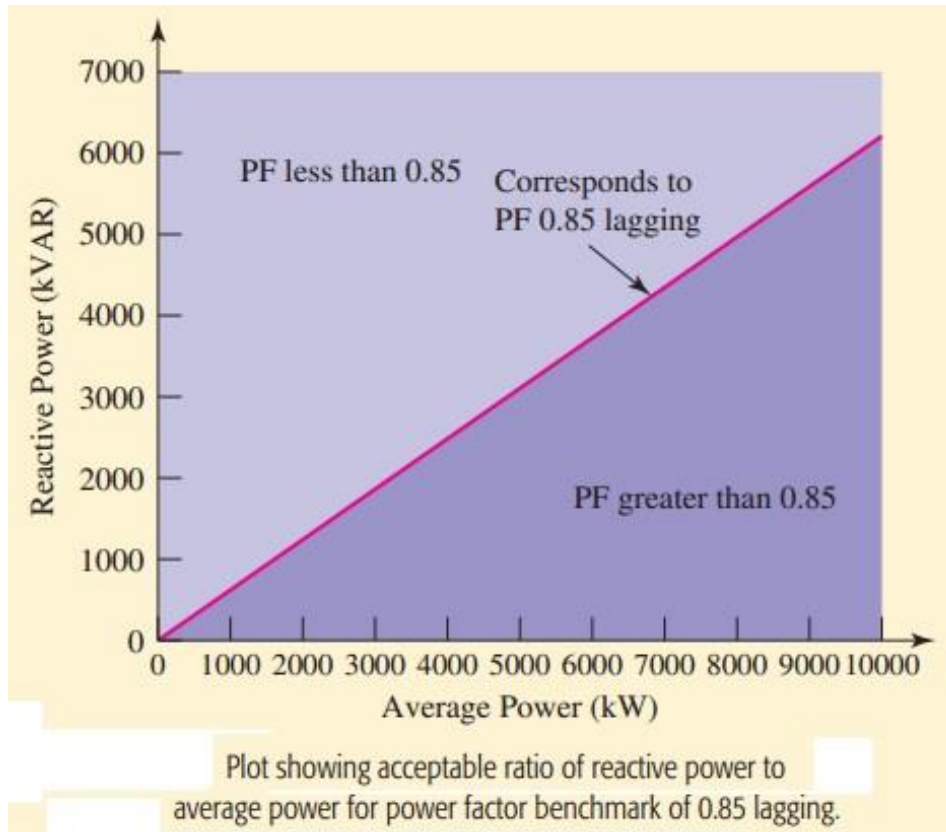

4.5 Complex Power- Công suất phức

Exercise 3.9

The voltage across a load is $v(t) = 60 \cos(\omega t - 10^\circ)$ V and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ)$ A.

Find:

- (a) the complex and apparent powers,
- (b) the real and reactive powers,
- (c) the power factor and the load impedance.

4.5 Complex Power- Công suất phức

Solution: (a) the complex and apparent powers:

$$\mathbf{V}_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ, \quad \mathbf{I}_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle +50^\circ$$

The complex power is

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \left(\frac{60}{\sqrt{2}} \angle -10^\circ \right) \left(\frac{1.5}{\sqrt{2}} \angle -50^\circ \right) = 45 \angle -60^\circ \text{ VA}$$

The apparent power is $S = |\mathbf{S}| = 45 \text{ VA}$

(b) the real and reactive powers:

$$\mathbf{S} = 45 \angle -60^\circ = 45[\cos(-60^\circ) + j \sin(-60^\circ)] = 22.5 - j38.97$$

$$P = 22.5 \text{ W (Real powers)} \quad Q = -38.97 \text{ VAR (Reactive powers)}$$

(c) the power factor and the load impedance: $\text{pf} = \cos(-60^\circ) = 0.5 \text{ (leading)}$

It is leading, because the reactive power is negative. The load impedance is

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{60 \angle -10^\circ}{1.5 \angle +50^\circ} = 40 \angle -60^\circ \Omega$$

which is a capacitive impedance.

4.5 Complex Power- Công suất phức

HOMEWORK 3.7

For a load, $V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$, $I_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$. Determine: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

Answer: (a) $44 \angle 70^\circ \text{ VA}$, 44 VA , (b) 15.05 W , 41.35 VAR , (c) 0.342 lagging, $94.06 + j258.4 \Omega$.

4.6 Polyphase circuits – Mạch đa pha

WHY THREE PHASE SYSTEM?

- ALL electric power system in the world used 3-phase system to **GENERATE, TRANSMIT** and **DISTRIBUTE**
- Instantaneous power is constant – thus smoother rotation of electrical machines
- More economical than single phase – less wire for the same power transfer


4.7 Single-Phase Three-Wire Systems

Balanced 3-phase systems



Single-phase two-wire system:

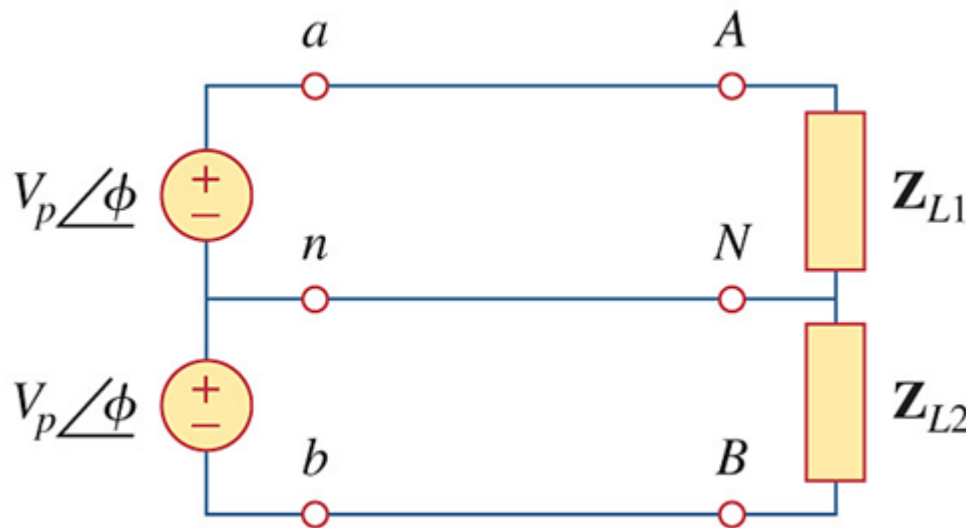- Single source connected to a load using two-wire system




Single-phase three-wire system:

- Two sources connected to two loads using three-wire system
- Sources have **EQUAL magnitude** and are **IN PHASE**


4.7 Single-Phase Three-Wire Systems

Balanced Two-phase three-wire system:

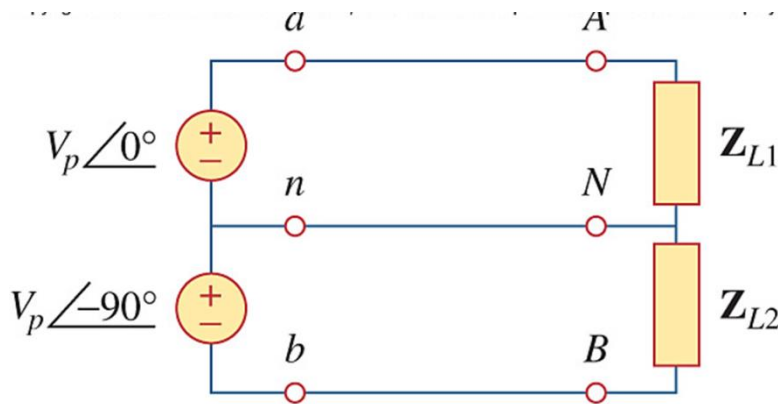

- Two sources connected to two loads using three-wire system
- Sources have EQUAL frequency but DIFFERENT phases


Balanced Three-phase four-wire system:

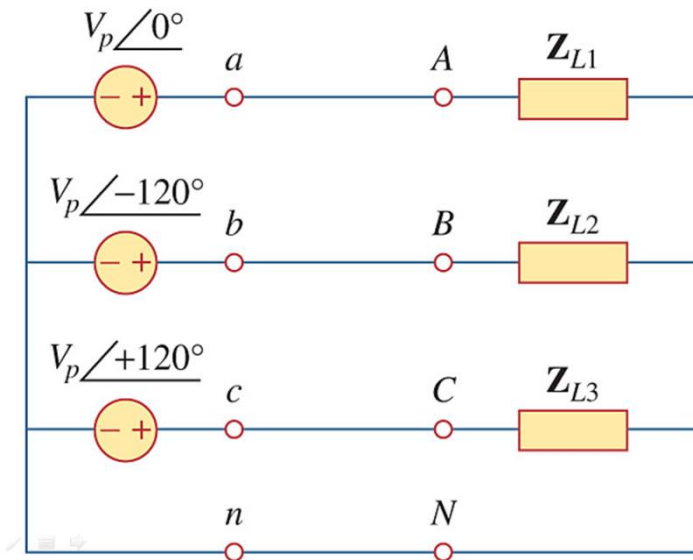

- Three sources connected to 3 loads using four-wire system
- Sources have EQUAL frequency but DIFFERENT phases

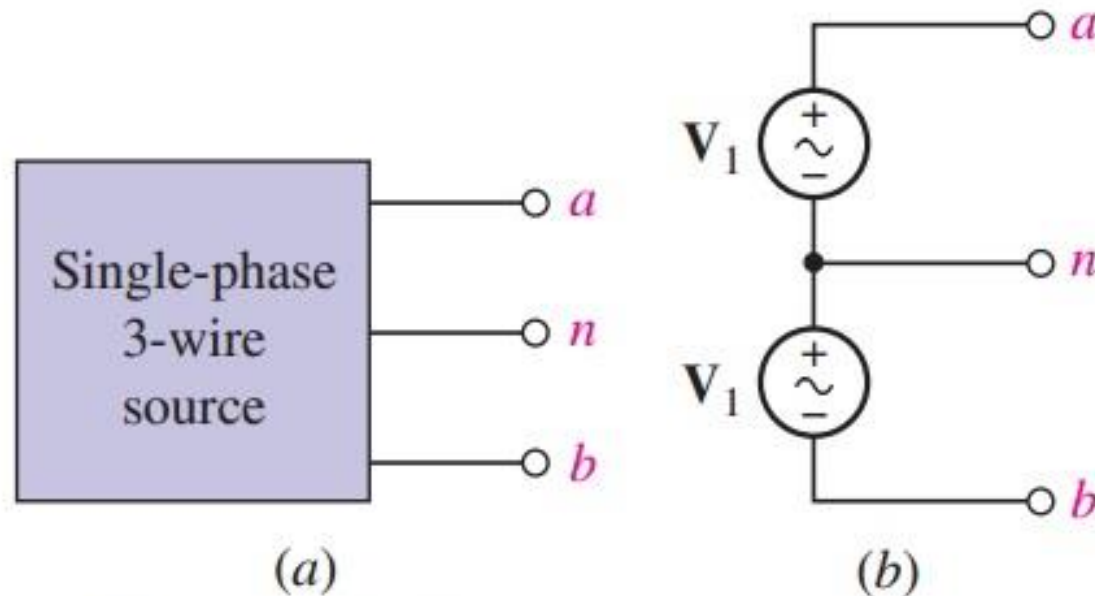4.7 Single-Phase Three-Wire Systems


A **single-phase three-wire source** is defined as a source having three output terminals, such as a , n , and b as shown in Figure, at which the phasor voltages V_{an} and V_{nb} are equal



(a) A single-phase three-wire source.

(b) The representation of a single-phase three-wire source by two identical voltage sources.

4.7 Single-Phase Three-Wire Systems

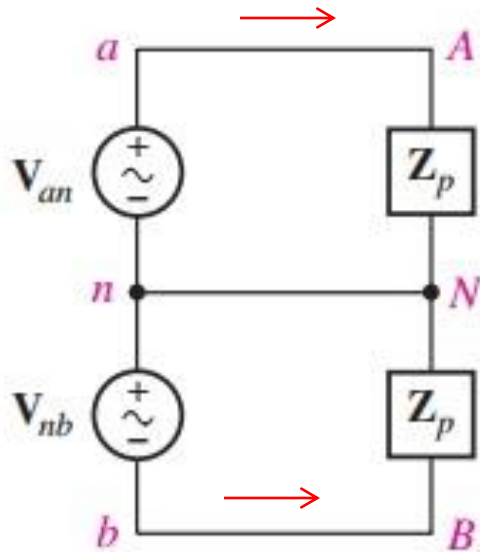

A simple single-phase three-wire system. The two loads are identical, and the neutral current is zero.

$$V_{an} = V_{nb}$$

$$I_{aA} = \frac{V_{an}}{Z_p} = I_{Bb} = \frac{V_{nb}}{Z_p}$$


$$I_{nN} = I_{Bb} + I_{Aa} = I_{Bb} - I_{aA} = 0$$

Thus there is no current in the neutral wire, and it could be removed without changing any current or voltage in the system. This result is achieved through the equality of the two loads and of the two sources.

4.7 Single-Phase Three-Wire Systems

Balanced 3-phase systems

Generation of 3-phase voltage: Generator

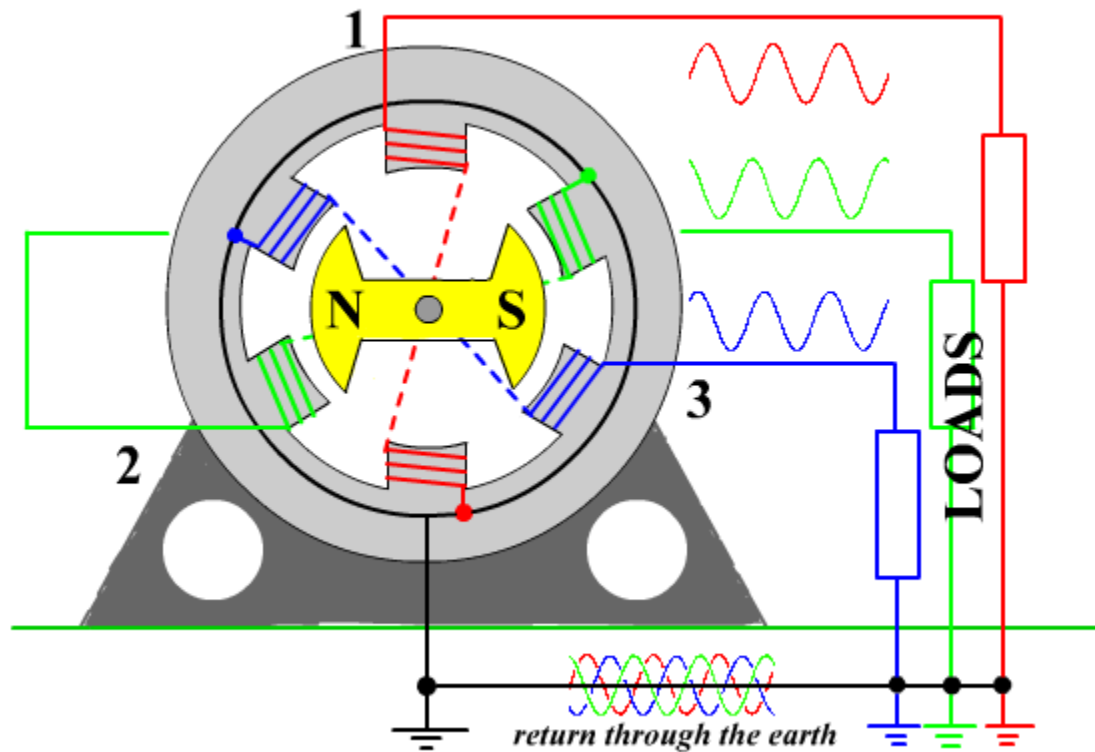


4.7 Single-Phase Three-Wire Systems

Balanced 3-phase systems

Generation, Transmission and Distribution


Basic Structure of the Electric System

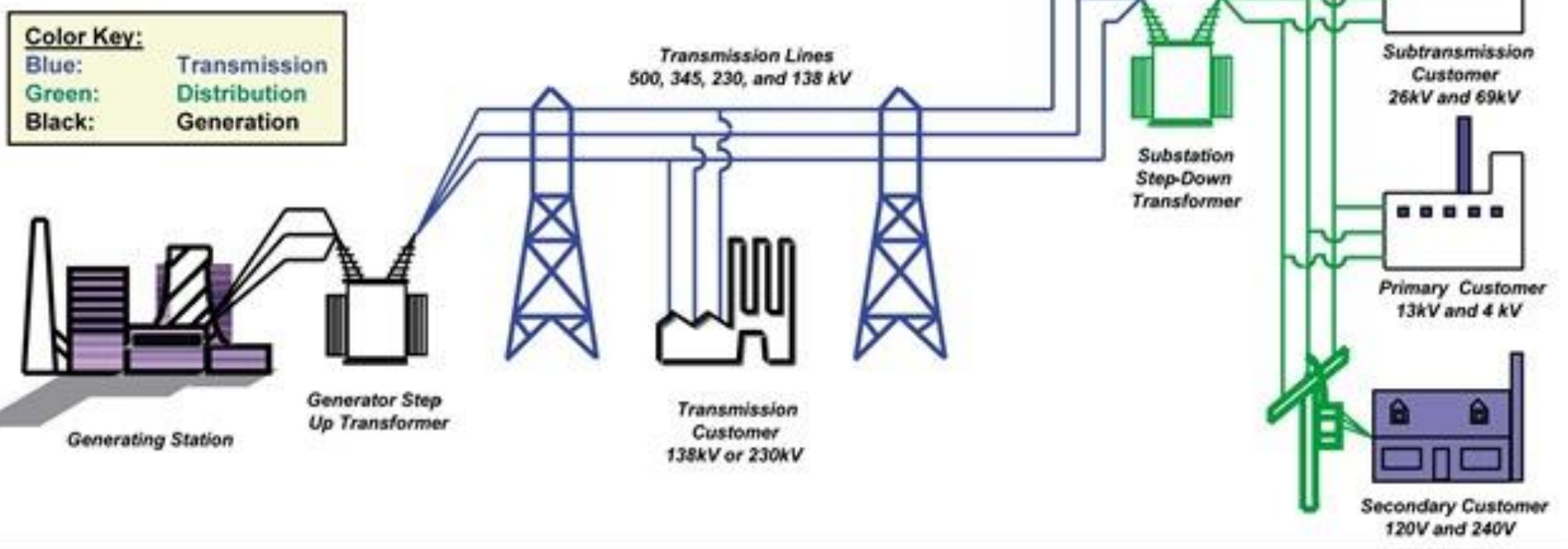

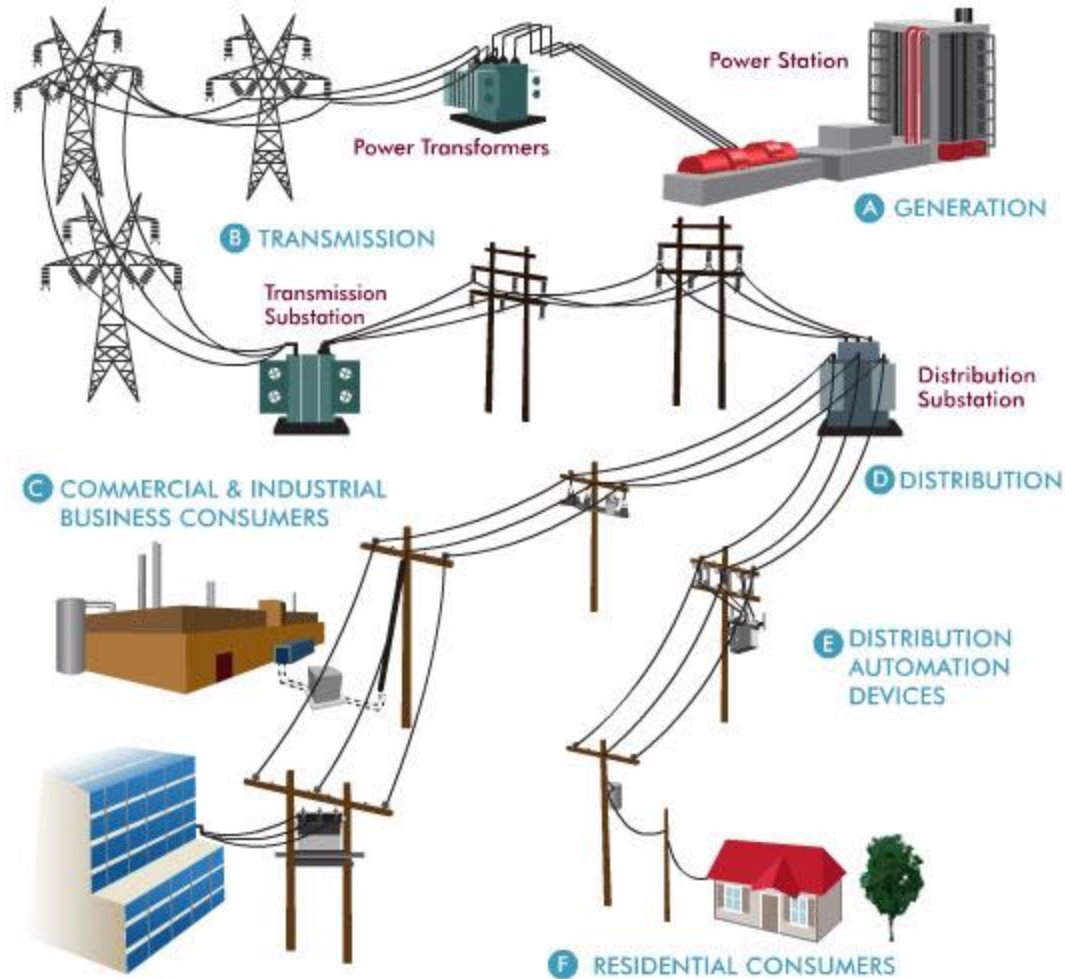4.7 Single-Phase Three-Wire Systems

Balanced 3-phase systems

Generation, Transmission and Distribution



4.8 Three-Phase Y-Y Connection

Balanced 3-phase systems

Y and Δ connections

Balanced 3-phase systems can be considered as 3 equal single phase voltage sources connected either as Y or Delta (Δ) to 3 single three loads connected as either Y or Δ

SOURCE CONNECTIONS

Y connected source

Δ connected source

LOAD CONNECTIONS

Y connected load

Δ connected load

Y-Y

Y- Δ

Δ -Y


Δ - Δ

4.8 Three-Phase Y-Y Connection

Balanced 3-phase systems

SOURCE CONNECTIONS


Source : Y connection

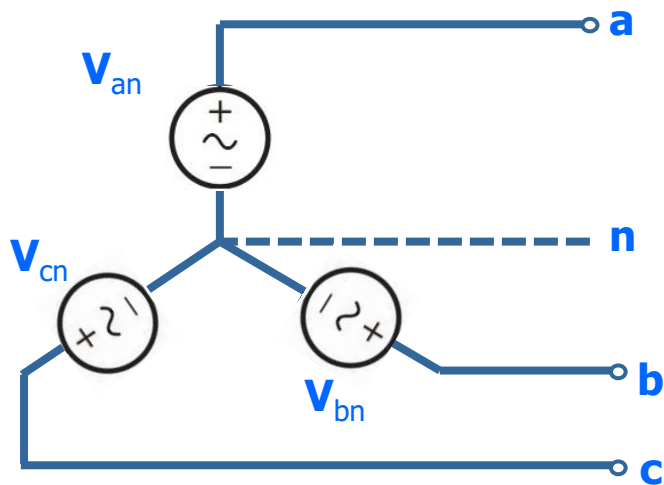

$$v_{an}(t) = \sqrt{2}V_p \cos(\omega t) \Rightarrow V_{an} = V_p \angle 0^\circ$$


$$v_{bn}(t) = \sqrt{2}V_p \cos(\omega t - 120^\circ) \Rightarrow V_{bn} = V_p \angle -120^\circ$$
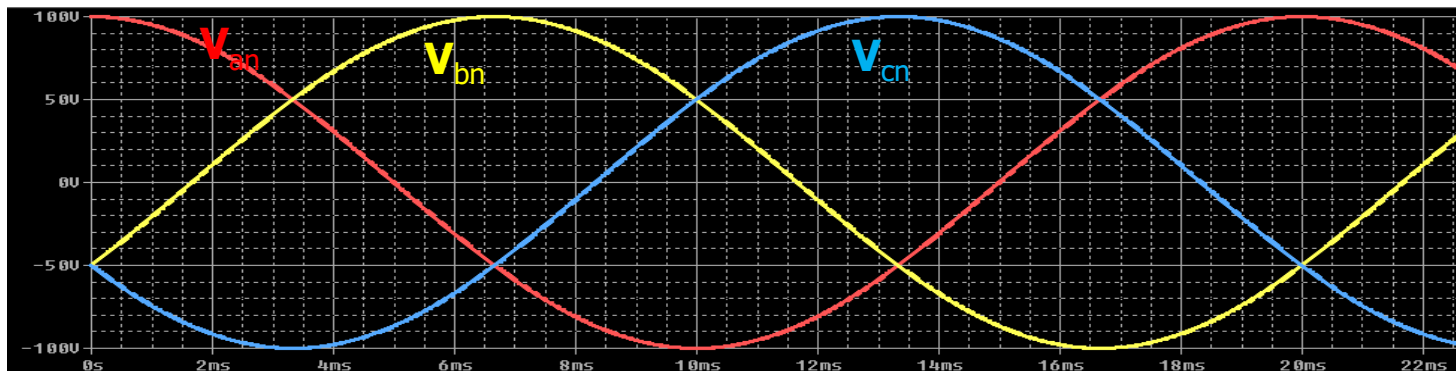
$$v_{cn}(t) = \sqrt{2}V_p \cos(\omega t + 120^\circ) \Rightarrow V_{cn} = V_p \angle 120^\circ$$




4.8 Three-Phase Y-Y Connection

Generation of 3-phase voltage: Generator

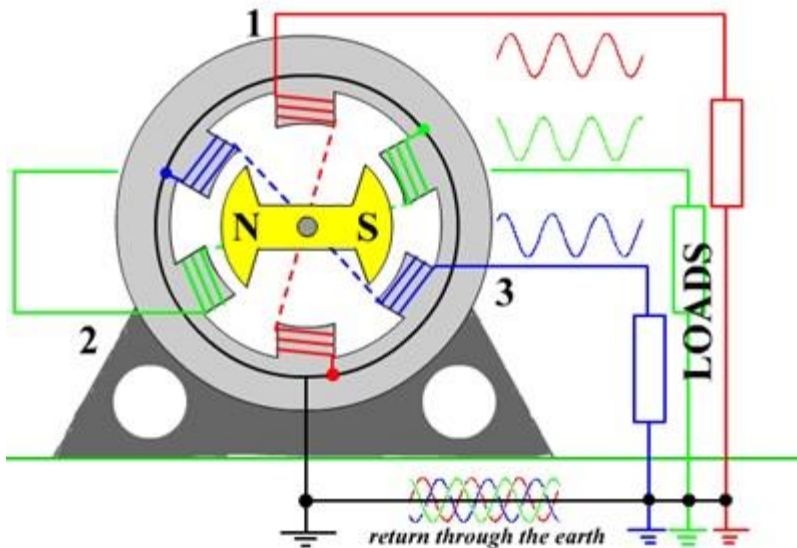

An example set of three voltages

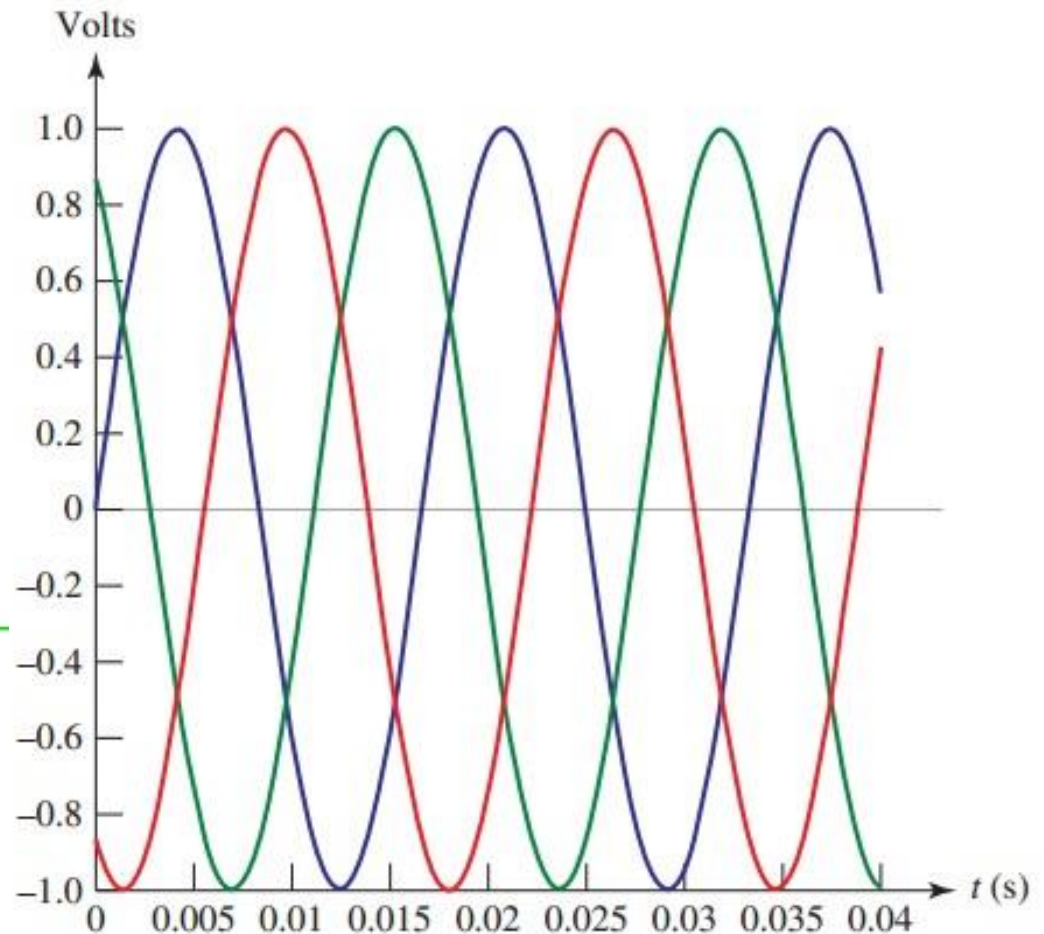


An example set of three voltages, each of which is 120° out of phase with the other two. As can be seen, only one of the voltages is zero at any particular instant.

4.8 Three-Phase Y-Y Connection

Balanced 3-phase systems

Source : Y connection

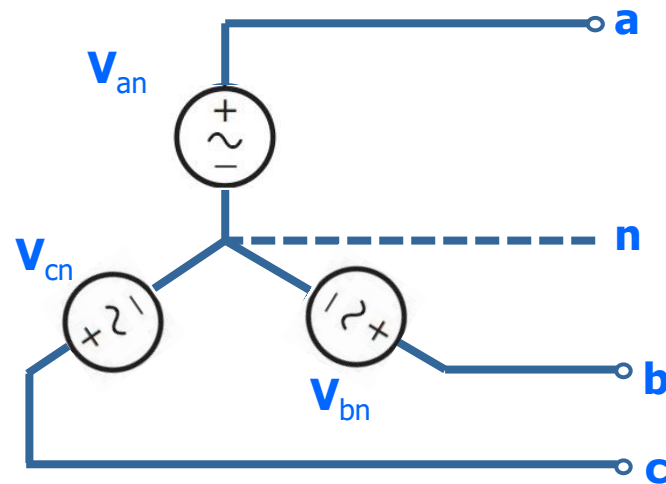


$$v_{an}(t) = \sqrt{2}V_p \cos(\omega t) \Rightarrow V_{an} = V_p \angle 0^\circ$$

$$v_{bn}(t) = \sqrt{2}V_p \cos(\omega t - 120^\circ) \Rightarrow V_{bn} = V_p \angle -120^\circ$$

$$v_{cn}(t) = \sqrt{2}V_p \cos(\omega t + 120^\circ) \Rightarrow V_{cn} = V_p \angle 120^\circ$$

4.8 Three-Phase Y-Y Connection

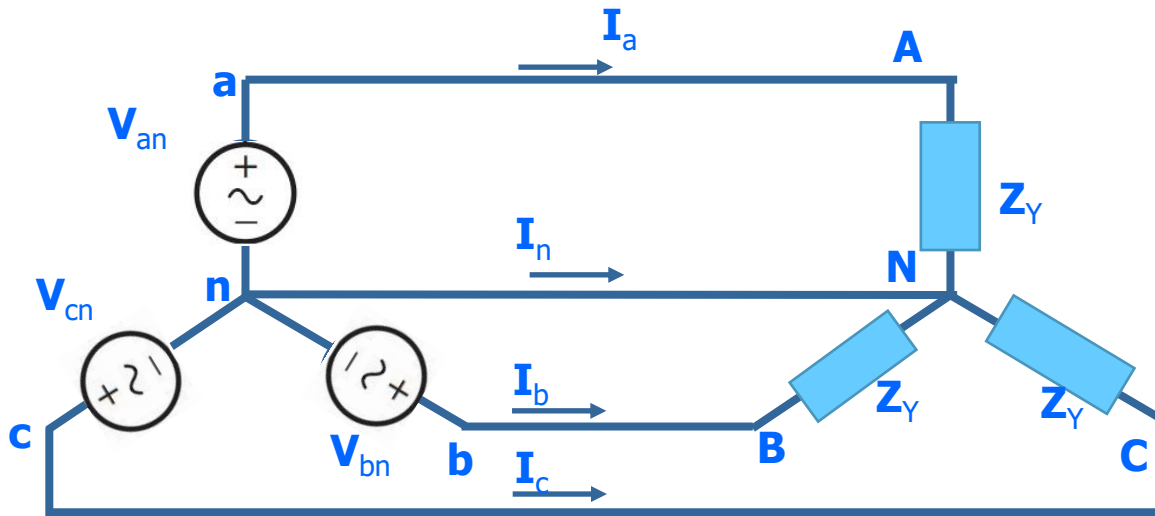

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle 120^\circ$$

**Phase
voltages**

$$I_a = \frac{V_p \angle 0^\circ}{Z_Y}$$

$$I_b = \frac{V_p \angle -120^\circ}{Z_Y}$$

$$I_c = \frac{V_p \angle 120^\circ}{Z_Y}$$

$$\therefore I_a + I_b + I_c = I_n = 0$$

**line
currents**

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} \\ &= V_p \angle 0^\circ + V_p \angle 60^\circ \\ &= \sqrt{3} V_p \angle 30^\circ \end{aligned}$$


$$\begin{aligned} V_{bc} &= V_{bn} + V_{nc} \\ &= \sqrt{3} V_p \angle -90^\circ \end{aligned}$$

$$\begin{aligned} V_{ca} &= V_{cn} + V_{na} \\ &= \sqrt{3} V_p \angle 150^\circ \end{aligned}$$

**line-line
voltages
OR
Line
voltages**

The wire connecting n and N can be removed !

4.8 Three-Phase Δ - Δ Connection

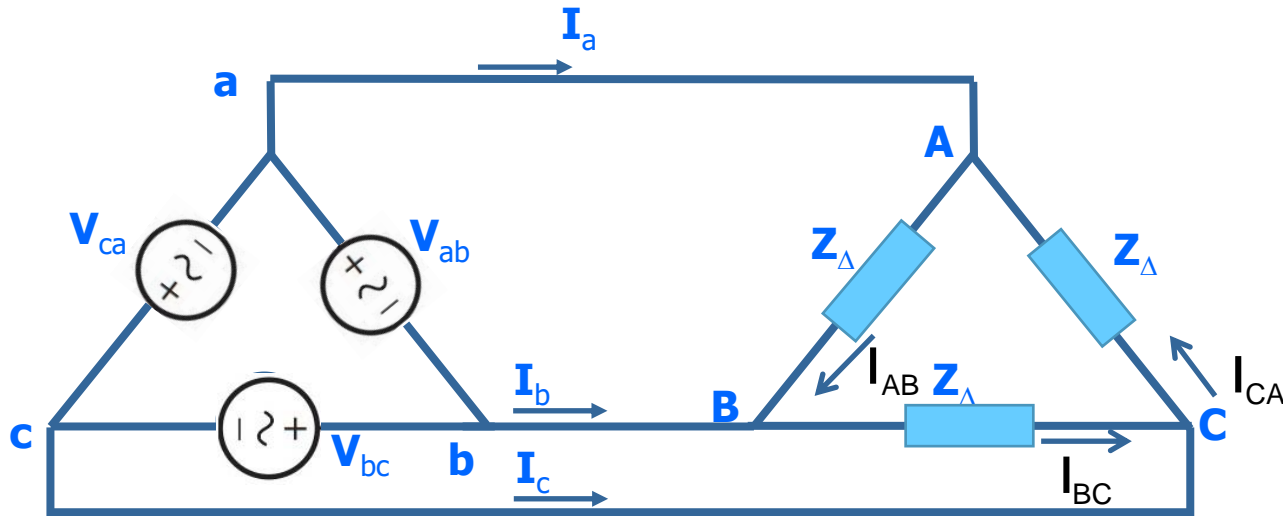

$$V_{ab} = V_p \angle 0^\circ$$

$$V_{bc} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle 120^\circ$$

$$V_{ab} = V_{AB}$$

$$V_{bc} = V_{BC}$$

$$V_{ca} = V_{CA}$$

$$I_{AB} = \frac{V_{AB}}{Z_\Delta}$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta}$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta}$$

Using KCL,

Phase currents

$$\begin{aligned} I_a &= I_{AB} - I_{CA} \\ &= I_{AB}(1 - 1 \angle 120^\circ) \\ &= I_{AB} \sqrt{3} \angle -30^\circ \end{aligned}$$


$$\begin{aligned} I_b &= I_{BC} - I_{AB} \\ &= I_{BC}(1 - 1 \angle 120^\circ) \\ &= I_{BC} \sqrt{3} \angle -30^\circ \end{aligned}$$

$$I_c = I_{CA} \sqrt{3} \angle -30^\circ$$

line currents

4.9 Power Measurement

Power Measurement

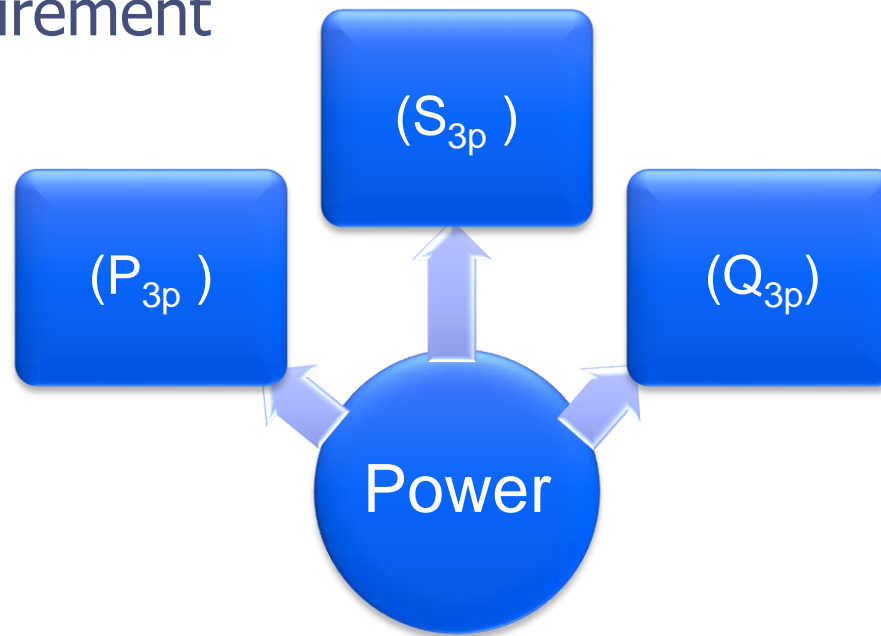

$$P_{3p} = U_A I_A \cos\varphi_A + U_B I_B \cos\varphi_B + U_C I_C \cos\varphi_C$$

$$Q_{3p} = U_A I_A \sin\varphi_A + U_B I_B \sin\varphi_B + U_C I_C \sin\varphi_C$$

$$S_{3p} = \sqrt{P_{3p}^2 + Q_{3p}^2}$$

